


Chapter 7: Flip-flops, Registers, Counters and a simple Processor

- Until now we have only considered combinational logic i.e. logic without memory where any change to an input directly effects the output.
- Simple example in figure 7.1 and 7.2

July 2000

Univ. of Stellenbosch - Digital Systems 144


212

 

July 2000

Figure 7.1 Control of an alarm system

213

 

July 2000

Figure 7.2 A simple memory element

214



7.1 Basic Latch (Afr: Grendel)

- Set (Afr: stel) and Reset (Afr: herstel) signals are required to change the state of a memory element.
- Example built with two NOR gates in figure 7.4 and 7.5
- Often called a SR latch.

July 2000

Univ. of Stellenbosch - Digital Systems 144

215

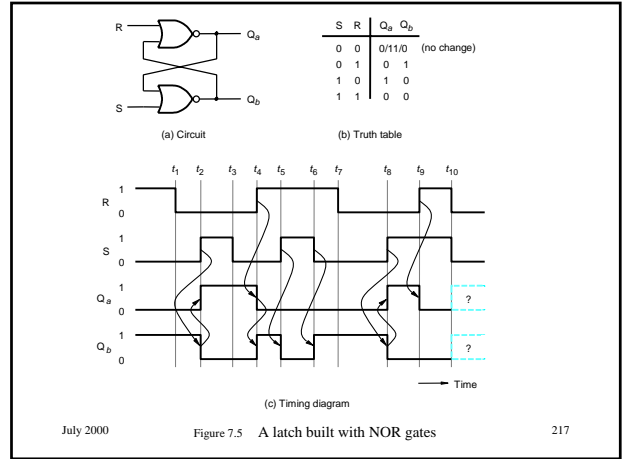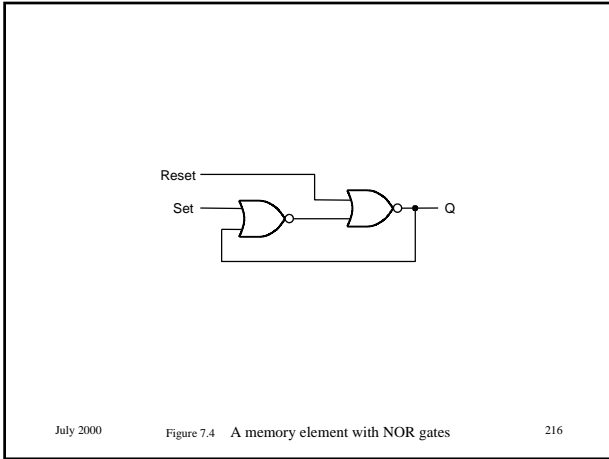


7.2 Gated SR latch

- We often need to isolate a latch from the inputs using a gate, enable or clock signal.
- In figure 7.6 S and R may change while clk is low (latch disabled).
- $Q(t) = Q(t+1)$


July 2000 218

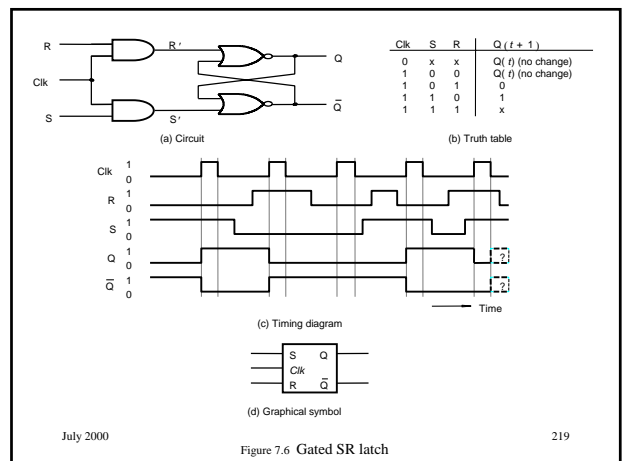Univ. of Stellenbosch - Digital Systems 144



 
7.2.1 Gated SR latch with NAND gates.

- NAND gates require fewer transistors to implement. Will therefore get preference.
- See figure 7.7



 7.3 Gated D Latch


- D Latch, D-type latch (Afr: D-tipe grendel)
- Figure 7.8.
- Data Latch – very useful for implementing Data memory.
- Level sensitive vs. edge triggered.
- Transparent latch.
- Data and load signals.




(a) Circuit

Clk	D	$Q(t+1)$
0	X	$Q(t)$
1	0	0
1	1	1

(b) Truth table

 

(c) Graphical symbol

 

(d) Timing diagram


7.3.1 Effects of Propagation Delays

- Setup and hold times
- Propagation delay times
- Figure 7.9

July 2000

Univ. of Stellenbosch - Digital Systems 144

224

 

July 2000

Figure 7.9 Setup and hold times

225

7.4 Master-Slave and Edge-Triggered D Flip-Flops

- In level sensitive latches the output will change with the input while the clock is active.
- Edge-triggered flip-flops only change the output at the edge of the clock.
- (Afr: Meester-slaaf en kantgesnellerde D-tipe wipkringe)

July 2000

Univ. of Stellenbosch - Digital Systems 144

226


7.4.1 Master-Slave D Flip-Flop

- In figure 7.10 the master flip-flop follows the input while the clock is high and the slave flip-flop follows the output of the master while the clock is low.
- The output only changes at the negative edge of the clock and is insensitive to the input value during the rest of the clock cycle.

July 2000

Univ. of Stellenbosch - Digital Systems 144


227

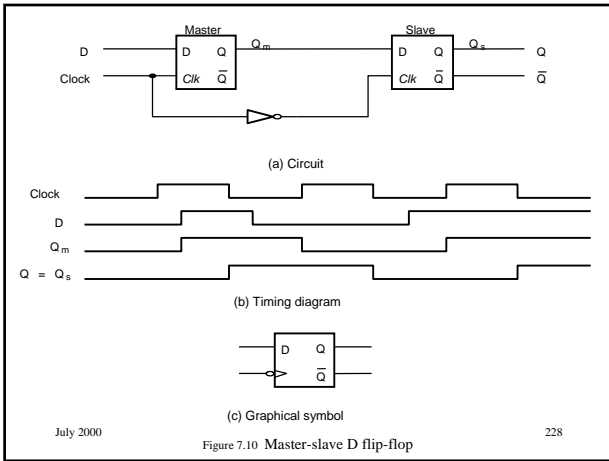

Level-sensitive vs. Edge-triggering

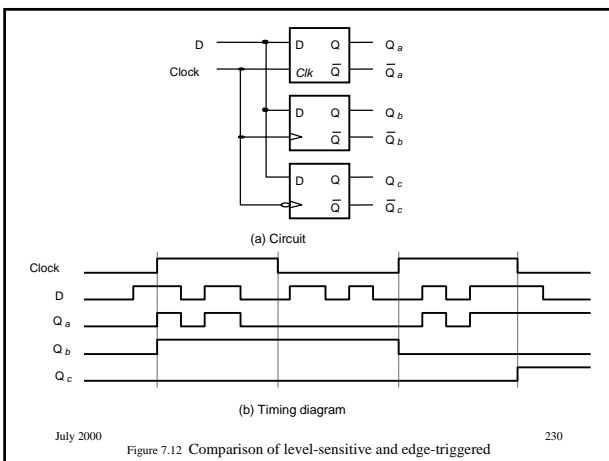- Example see figure 7.12


July 2000 Univ. of Stellenbosch - Digital Systems 144 229



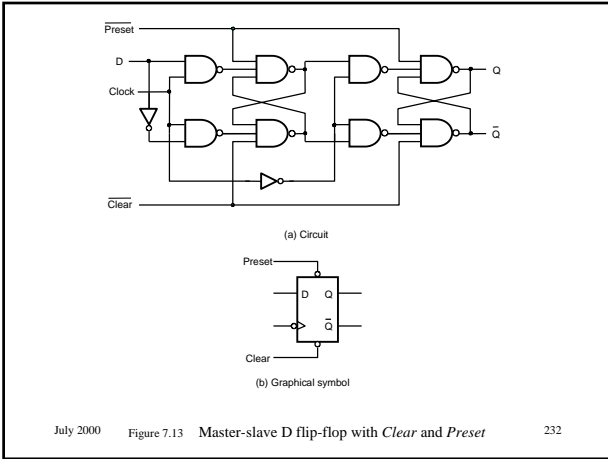7.4.3D Flip-Flops with Clear and Preset

- Preset and clear are asynchronous with the clock.
- Higher priority.
- Usually used to initialize a flip-flop after power is turned on.
- See figure 7.13.


July 2000 Univ. of Stellenbosch - Digital Systems 144 231



Synchronous reset

- See figure 7.15

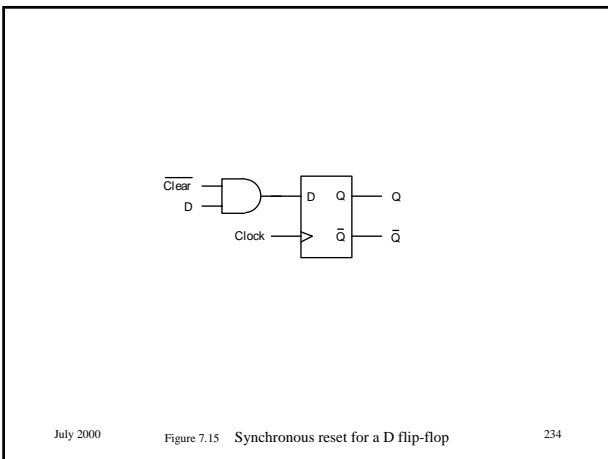
July 2000 Univ. of Stellenbosch - Digital Systems 144 233



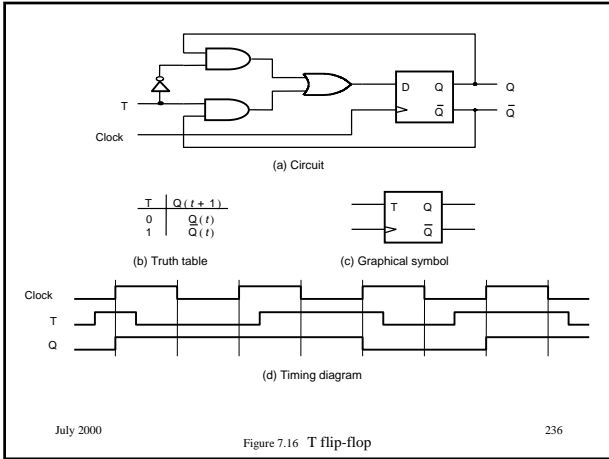7.5 T Flip-Flop

- Toggle means “going to the opposite state when a clock transition occurs”.
- Useful to build counters.
- See figure 7.16.


July 2000 Univ. of Stellenbosch - Digital Systems 144 235



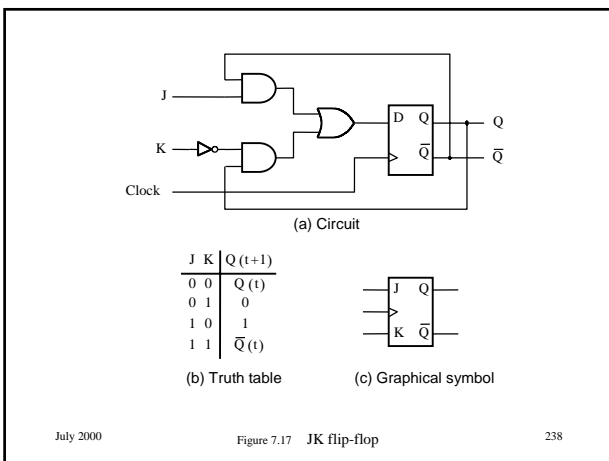7.6 JK Flip-Flop

- D input defined as $D = JQ' + K'Q$
- Combines behaviors of SR and T flip-flops
- Behaves as a SR flip-flop when $J = S$ and $K = R$ for all input values except $J = K = 1$. For the latter it behaves as a T flip-flop.
- See figure 7.17.

July 2000 Univ. of Stellenbosch - Digital Systems 144 237



7.7 Summary of Technology

- Basic Latch – two NOR gates or two NAND gates.
- Gated Latch (SR or D)
- Flip-Flop (changes state at clock transition)
 - Edge-triggered flip-flop
 - Master-slave flip-flop

July 2000 Univ. of Stellenbosch - Digital Systems 144 239

7.8 Registers

- Now moving from gate level to register level logic circuits.
- When a set of n identical flip-flops is used to store n bits, it is referred to as a *register*.
- **ALL REGISTERS RELY ON A SINGLE UNBUFFERED CLOCK AND THE INHERENT DELAY OF THE CIRCUITS.**

July 2000

Univ. of Stellenbosch - Digital Systems 144

240


7.8.1 Shift Register

- Shifts the bits in a register one position per clock pulse from left-to-right or from right-to-left.
- See figure 7.18.

July 2000

Univ. of Stellenbosch - Digital Systems 144

241

 

(a) Circuit

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

(b) A sample sequence

July 2000

Figure 7.18 A simple shift register

242


7.8.2 Parallel-Access Shift Register

- A shift register that can be loaded and read in parallel.
- Often used to convert parallel-to-serial and serial-to-parallel data streams.
- See figure 7.19.

July 2000

Univ. of Stellenbosch - Digital Systems 144

243

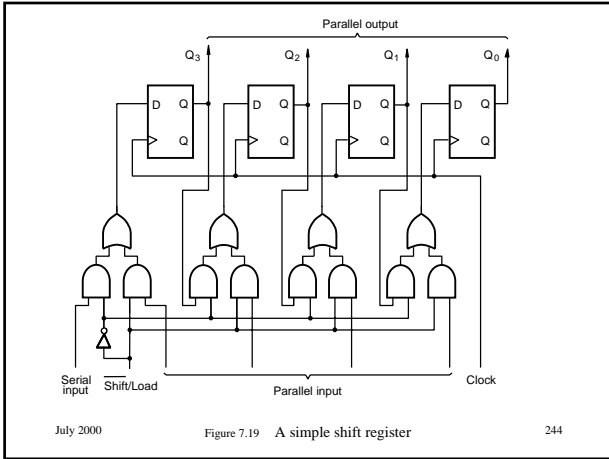

July 2000

Figure 7.19 A simple shift register

244

7.9 Counters

- Counters are circuits that add or subtract values by 1.
- Simpler circuits than full adders will suffice.
- Two main types:
 - Asynchronous or ripple counters.
 - Synchronous counters.

July 2000

Univ. of Stellenbosch - Digital Systems 144

245


7.9.1 Asynchronous Counters

- Up-counter with T flip-flops (figure 7.20)
- Down counter with T flip-flops (figure 7.21)

July 2000

Univ. of Stellenbosch - Digital Systems 144


246

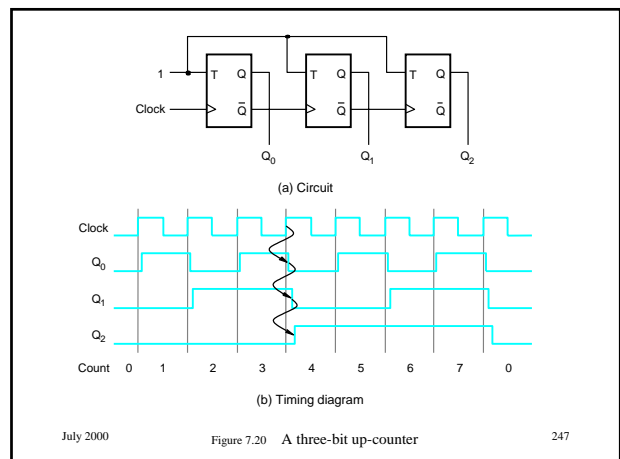

July 2000

Figure 7.20 A three-bit up-counter

247

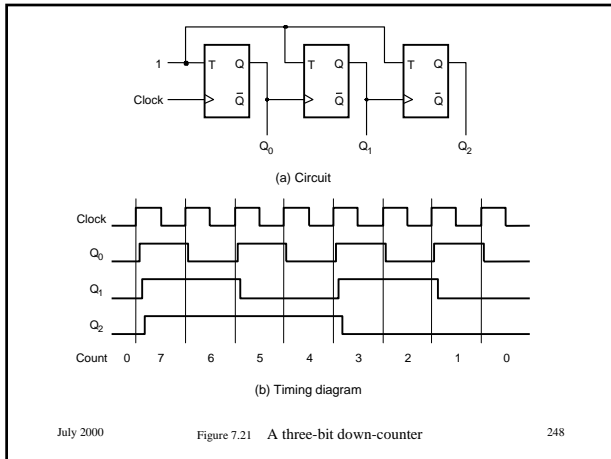

7.9.2 Synchronous Counters


- Synchronous Counters with T flip-flops
 - Observe pattern in table 7.1 resulting in:
 - $T_0 = 1$
 - $T_1 = Q_0$
 - $T_2 = Q_0Q_1$
 - $T_3 = Q_0Q_1Q_2$
 - $T_n = Q_0Q_1 \dots Q_{n-1}$
 - Implementation in figure 7.22
 - Note effect on speed of counter.
 - Enable and clear added in figure 7.23.


July 2000 Univ. of Stellenbosch - Digital Systems 144 249

Clock cycle	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0



Q₁ changes
Q₂ changes

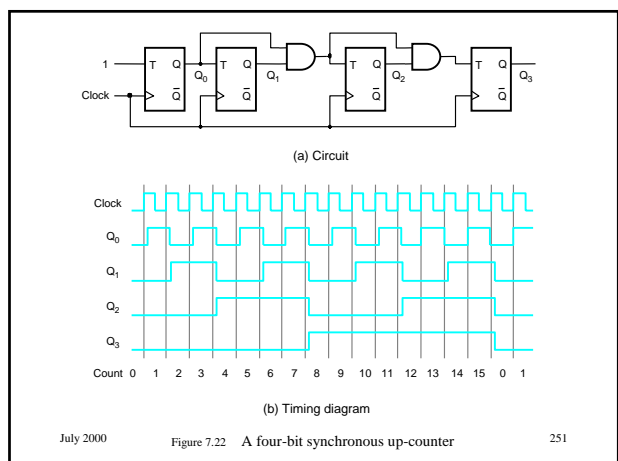July 2000 Table 7.1 Derivation of the synchronous up-counter 250



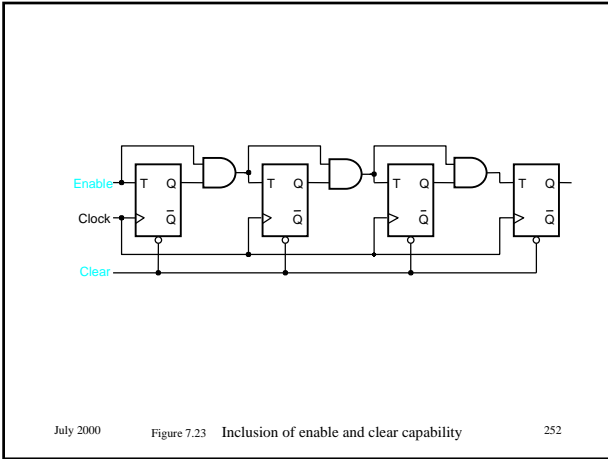

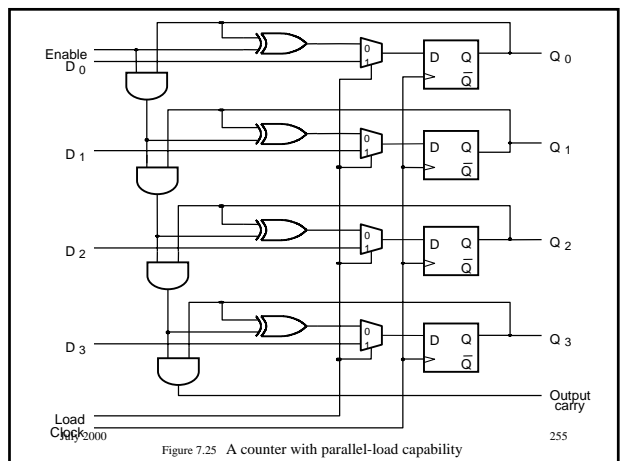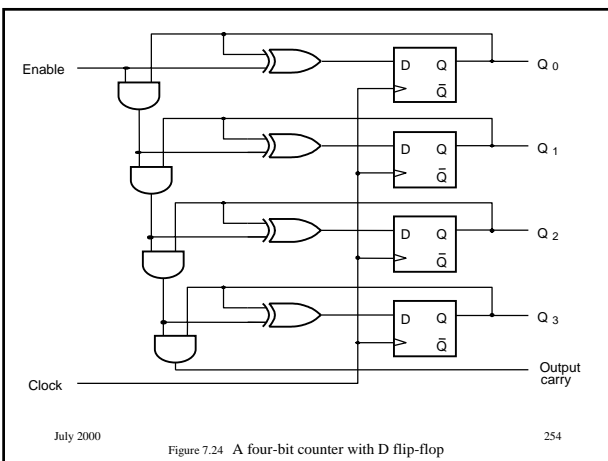- Synchronous counter with D flip-flops
 - Formal proof in chapter 8.
 - $D_0 = Q_0 \oplus \text{Enable}$
 - $D_1 = Q_1 \oplus Q_0 \text{ Enable}$
 - $D_2 = Q_2 \oplus Q_1 Q_0 \text{ Enable}$
 - See figure 7.24
 - 7.9.3 Counters with parallel load
 - See figure 7.25
- July 2000 Univ. of Stellenbosch - Digital Systems 144 253




7.10 Reset Synchronization

- Circuit in figure 7.25 can be used to build a modulo-n counter. See figure 7.26 as an example of a modulo-6 counter using *synchronous load*.
- The circuit in figure 7.27 uses asynchronous reset inputs, but has a potential problem of cutting state 5 short – not recommended!


July 2000

Univ. of Stellenbosch - Digital Systems 144

256

 

(a) Circuit

 


(b) Timing diagram


July 2000

Figure 7.26 A modulo-6 counter with synchronous reset

257

 

(a) Circuit

 

(b) Timing diagram

July 2000

Figure 7.27 A modulo-6 counter with asynchronous reset

258




7.11 Other types of counters

- 7.11.1 BCD counter (figure 7.28)
 - Counts decimal
- 7.11.2 Ring counter (figure 7.29)
 - One hot code
- 7.11.3 Johnson counter (figure 7.30)
 - Only one bit changes at a time

July 2000

Univ. of Stellenbosch - Digital Systems 144

259

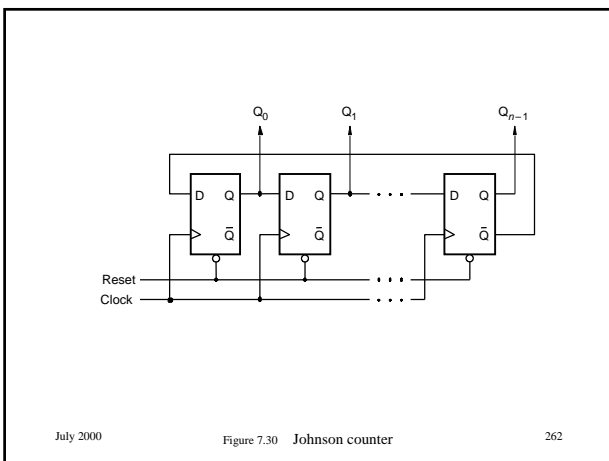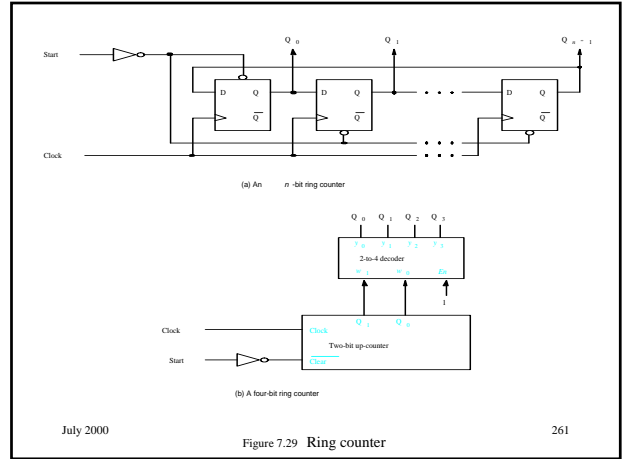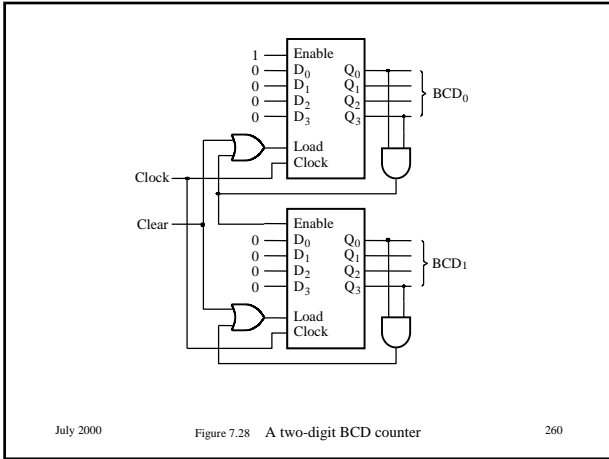

7.11.4 Remarks on counter design

- A number of “intuitive” counter designs have been presented in this chapter.
- A more general approach will be discussed in the next chapter.

July 2000 263

Univ. of Stellenbosch - Digital Systems 144


Rest of chapter 7

- The rest of chapter 6 will not be tested in the examination.
- Some concepts are discussed in order to give the students a broader *system* perspective of the digital building blocks are typically used in building more complex digital systems such as computers.

July 2000

Univ. of Stellenbosch - Digital Systems 144

264

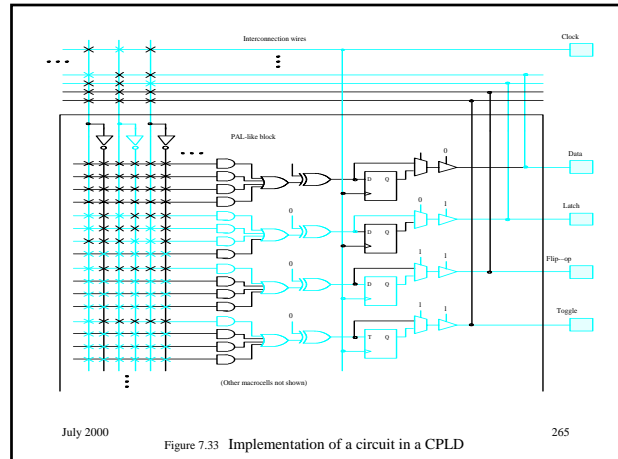

July 2000

Figure 7.33 Implementation of a circuit in a CPLD

265

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN  STD_LOGIC ;
          Q                 : OUT STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
    
```

July 2000

Figure 7.40 D flip-flop with asynchronous reset

266

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY reg8 IS
    PORT ( D : IN  STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, Clock : IN  STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END reg8 ;

ARCHITECTURE Behavior OF reg8 IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= "00000000" ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
    
```

July 2000 Figure 7.46

Code for an eight-bit register with asynchronous clear

267

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, Resetn, E :IN  STD_LOGIC ;
          Q :OUT  STD_LOGIC_VECTOR (3 DOWNTO 0));
END upcount ;

ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF E = '1' THEN
                Count <= Count + 1 ;
            ELSE
                Count <= Count ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;

```

July 2000 Figure 7.53 Code for a four-bit up-counter 268

```


LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY upcount IS
    PORT ( R : IN  INTEGER RANGE 0 TO 15 ;
          Clock, Resetn, L : IN  STD_LOGIC ;
          Q : BUFFER INTEGER RANGE 0 TO 15 ) ;
END upcount ;


ARCHITECTURE Behavior OF upcount IS
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Q <= 0 ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                Q <= Q + 1 ;
            END IF ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

Figure 7.54 A four-bit counter with parallel load, using INTEGER signals 269

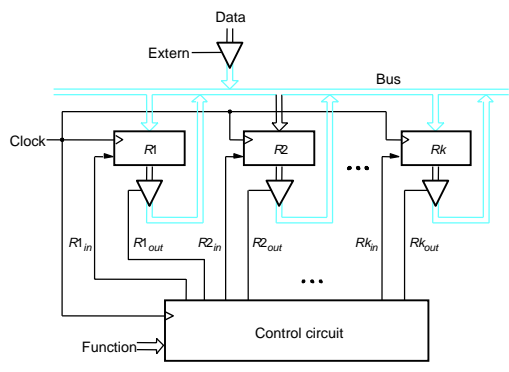

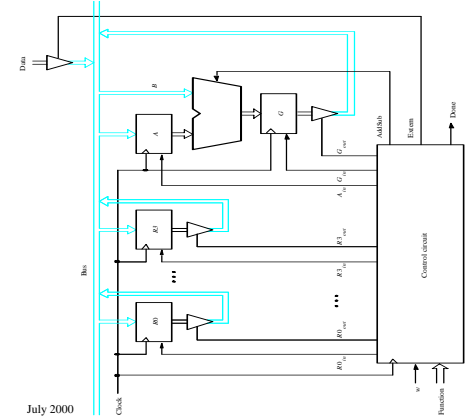July 2000 Figure 7.56 A digital system with k registers 270




July 2000 Figure 7.70 A digital system that implements a simple processor 271

Operation	Function performed
Load $Rx, Data$	$Rx \leftarrow Data$
Move Rx, Ry	$Rx \leftarrow [Ry]$
Add Rx, Ry	$Rx \leftarrow [Rx] + [Ry]$
Sub Rx, Ry	$Rx \leftarrow [Rx] - [Ry]$

July 2000

Table 7.2 Operations performed in the processor


272

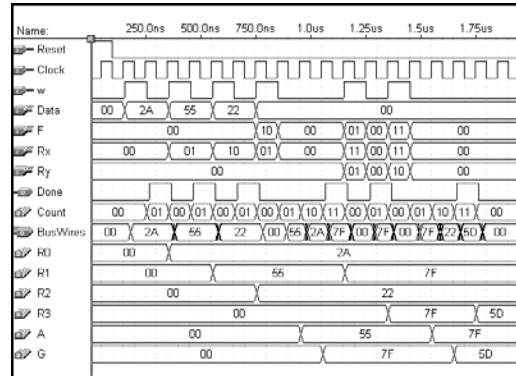

July 2000

Figure 7.76 Timing simulation of the processor

273

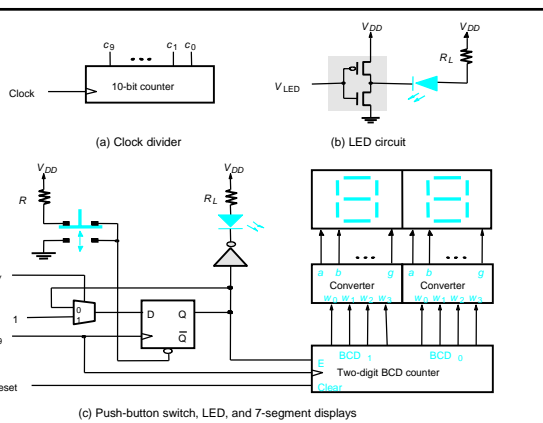

July 2000

Figure 7.77 A reaction-timer circuit

274