


Chapter 8 Synchronous Sequential Circuits

- Finite State Machine (FSM) (Afr: toestand masjien)
- Combination of combinatorial and sequential logic. Mealy and Moore types.
- Digital control circuits.
- See figure 8.1.

July 2000

Univ. of Stellenbosch - Digital Systems 144

275

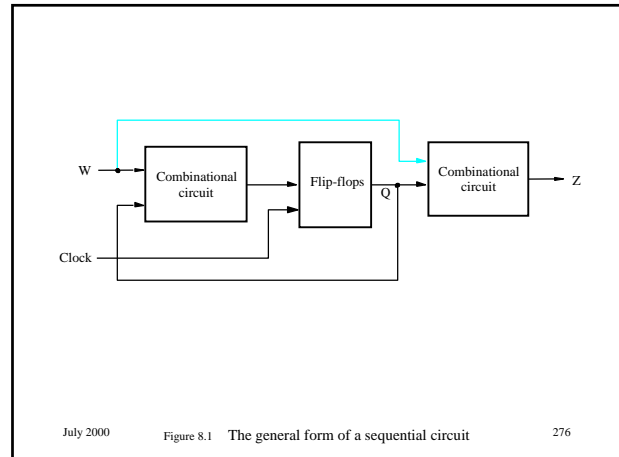

July 2000

Figure 8.1 The general form of a sequential circuit

276

8.1 Basic Design Steps

- Example:
 - A circuit has 1 input w and one output z .
 - Use positive edge clock.
 - $z = 1$ if during two immediate preceding clock cycles the input w was equal to 1. Otherwise $z = 0$.
 - See figure 8.2.

July 2000

Univ. of Stellenbosch - Digital Systems 144

277

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

July 2000

Figure 8.2 Sequences of input and output signals

278


8.1.1 State diagram (Afr: Toestanddiagram)

- A designer maps the descriptive specification onto a state diagram.
- Circles represent states (Afr: toestande) and arcs (Afr: boeë) represent transitions (Afr: oorgange of tsiensies) from one state to another.
- Starting state after reset.
- See figure 8.3.

July 2000

Univ. of Stellenbosch - Digital Systems 144

279

 

July 2000

Figure 8.3 State diagram of a simple sequential circuit

280

8.1.2 State Tables (Afr: Toestandtabel)

- A State Table tabulates Next States as a function all possible Present States and the inputs to the circuit.
- The State Machine moves from the Present State to Next State after each clock transition.
- See figure 8.4.

July 2000

Univ. of Stellenbosch - Digital
Systems 144

281

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1

July 2000

Figure 8.4 State table

282


8.1.3 State Assignment

- In an implementation each State is represented by a particular valuation (combination of values) of *State Variables*.
- Each *state variable* is implemented in the form of a *flip-flop*.
- See figure 8.5.

July 2000

Univ. of Stellenbosch - Digital
Systems 144

283

 

July 2000

Figure 8.5 A general sequential circuit

284

State-assignment table

- Similar to the state table, but with state names replaced by state variables.
- y_1 and y_2 are called present-state variables.
- Y_1 and Y_2 are called next-state variables.
- Note don't care state in figure 8.6.

July 2000

Univ. of Stellenbosch - Digital
Systems 144

285

Present state	Next state		Output z
	$w = 0$	$w = 1$	
$y_2 y_1$	$Y_2 Y_1$	$Y_2 Y_1$	
A	00	01	0
B	01	10	0
C	10	10	1
	11	dd	d

July 2000

Figure 8.6 A State-assigned table

286



8.1.4 Choice of flip-flops and Derivation of Next-State and Output Expressions

- Using D-type flip-flops is easy and straight forward, because the input is transferred unchanged to the output.
- See figures 8.7 and 8.8 for implementation.

July 2000

Univ. of Stellenbosch - Digital Systems 144

287

 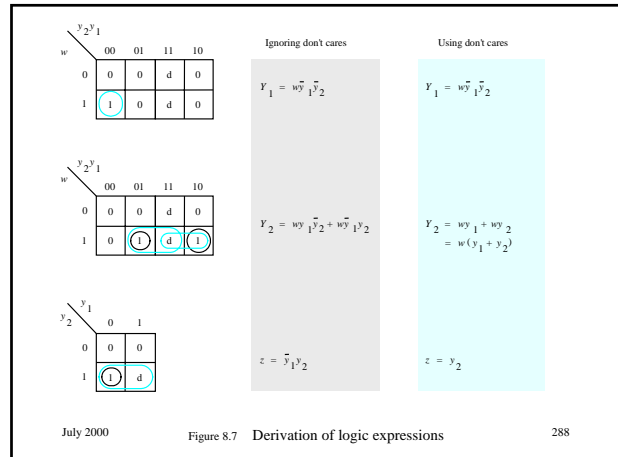

July 2000

Figure 8.8 Sequential circuit

289


8.1.5 Timing diagram

- Figure 8.9 shows the timing diagram, with delays, for the above example.
- (Students make sure you understand this detail.)

July 2000

Univ. of Stellenbosch - Digital Systems 144

290

 

July 2000

Figure 8.9 Timing diagram

291

8.1.6 Summary of design steps

- Obtain specification.
- Derive state diagram (engineering skill!).
- Create state table.
- Minimize states (later).
- State assignment.
- Choose flip-flops.
- Implement circuit.

July 2000

Univ. of Stellenbosch - Digital Systems 144

292


Example 8.1

- A slightly more complex example of a *control circuit*.
- A typical instruction in a computer is to swap the values of two registers via a three-state bus.
- See figure 7.56 and 7.57.

July 2000

Univ. of Stellenbosch - Digital Systems 144

293

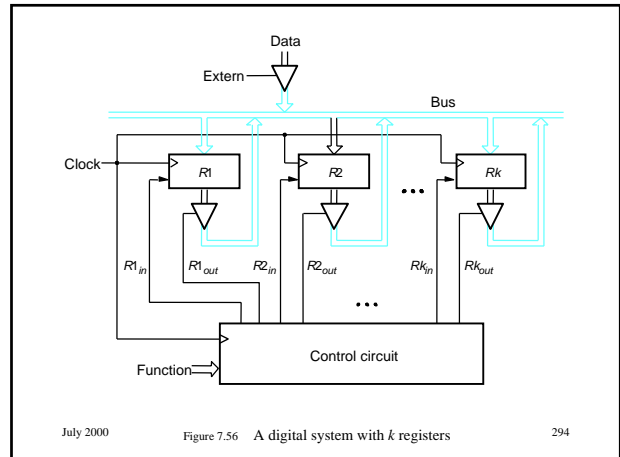

July 2000

Figure 7.56 A digital system with k registers

294


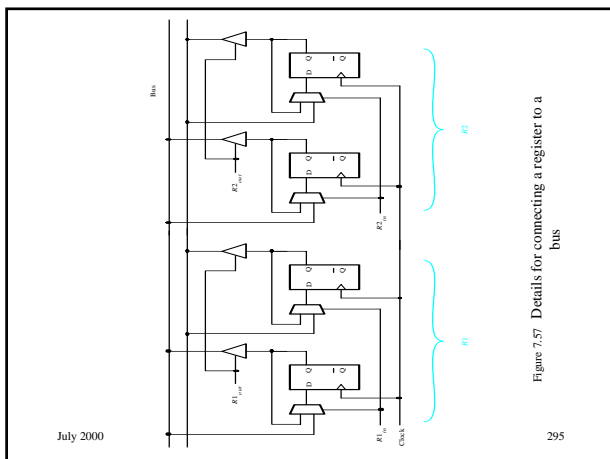


Figure 7.57 Details for connecting a register to a bus

July 2000


295

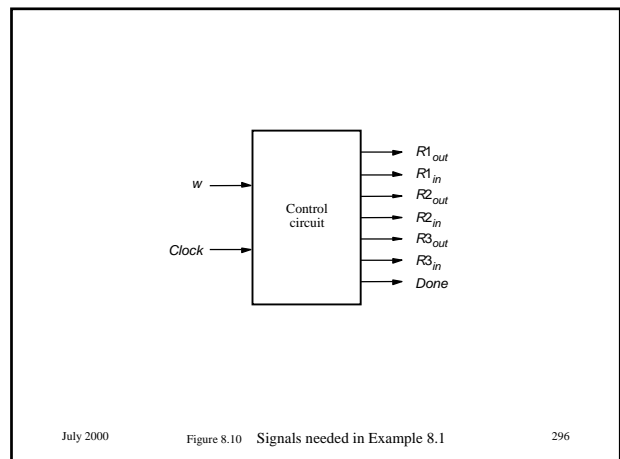

July 2000

Figure 8.10 Signals needed in Example 8.1

296

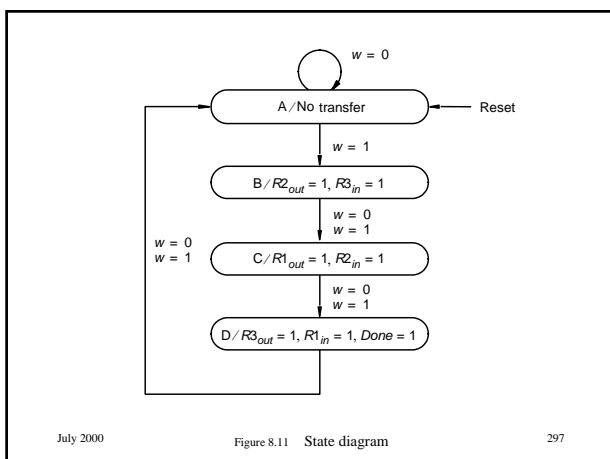

July 2000

Figure 8.11 State diagram

297

Present state	Next state		Outputs						
	w = 0	w = 1	R1 _{out}	R1 _{in}	R2 _{out}	R2 _{in}	R3 _{out}	R3 _{in}	Done
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

July 2000

Figure 8.12 State table


298

Present state	Nextstate		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
	y_2y_1	Y_2Y_1							
A	00	01	0	0	0	0	0	0	0
B	01	10	0	0	1	0	0	1	0
C	10	11	1	0	0	1	0	0	0
D	11	00	0	1	0	0	1	0	1

July 2000

Figure 8.13 State-assigned table


299

 

July 2000

Figure 8.14 Derivation of next-state expressions

300

 

July 2000

Figure 8.15 Sequential circuit

301

8.2 State assignment problem

- Alternate assignment of values to states can lead to simpler designs, but there is no formal procedure.
- CAD tools use proprietary heuristic techniques.
- See first example in figures 8.16 and 8.17.

July 2000

Univ. of Stellenbosch - Digital Systems 144


302

Present state	Next state		Output	
	$w = 0$	$w = 1$		
	y_2y_1	Y_2Y_1	Y_2Y_1	z
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	dd	dd	d

July 2000

Figure 8.16 Improved state assignment

303

 

July 2000

Figure 8.17 Final circuit for the improved state assignment

304

8.2.1 One-hot encoding

- One-hot encoding can be used to represent states in stead of binary encoding as used up to now.
- Disadvantage: requires more flip-flops.
- Advantage: simpler output circuit.

July 2000

Univ. of Stellenbosch - Digital Systems 144

305

Present state	Nextstate		Output z
	w = 0	w = 1	
$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$	
A	001	010	0
B	010	100	0
C	100	001	1

July 2000

Figure 8.20 One-hot state assignment

306

Present state	Nextstate		Outputs						
	w = 0	w = 1	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	Done
$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$	$Y_3 Y_2 Y_1$							
A	001	0010	0	0	0	0	0	0	0
B	010	0100	0	0	1	0	0	1	0
C	0100	1000	1	0	0	1	0	0	0
D	1000	0001	0	1	0	0	1	0	1

July 2000

Figure 8.21 One-hot state assignment

307

8.3 Mealy State Model

- Moore model – output only a function of the present state.
- Mealy model – output a function of the present state *and* the input(s).
- Example: modification of previous example – see figures 8.22 to 8.26.
- NB. During present clock cycle the output is determined by the state from which the arc emanates and the input value on the arc.

July 2000

Univ. of Stellenbosch - Digital Systems 144


308

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
w:	0	1	0	1	1	0	1	1	1	0	1
z:	0	0	0	0	1	0	0	1	1	0	0

July 2000

Figure 8.22 Sequences of input and output signals

309

 

July 2000

Figure 8.23 State diagram

310

Present state	Next state		Output z	
	w = 0	w = 1	w = 0	w = 1
A	A	B	0	0
B	A	B	0	1

July 2000

Figure 8.24 State table


311

Present state	Next state		Output	
	w = 0	w = 1	w = 0	w = 1
y	Y	Y	z	z
A	0	1	0	0
B	1	1	0	1


July 2000

Figure 8.25 State-assigned table

312

 

(a) Circuit

 

(b) Timing diagram

July 2000

Figure 8.26 FSM implementation


313

- If the output pulse is to be delayed by one clock cycle, a D-type flip-flop can be added at the output (figure 8.27).
- This circuit is now equivalent to the one in figure 8.17 and to the original specification.


July 2000

Univ. of Stellenbosch - Digital Systems 144

314

 

(a) Circuit

 

(b) Timing diagram

July 2000

Figure 8.27 FSM implementation


315

- Figure 8.28 shows the second example in Mealy form.

July 2000

Univ. of Stellenbosch - Digital Systems 144

316

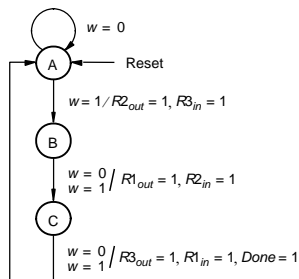

July 2000

Figure 8.28 State diagram for Example 8.4

317


8.7 Design of a Counter Using the Sequential circuit Approach

- 8.7.1 State diagram and state table for Modulo-8 counter (figure 8.60, 61)
- 8.7.2 State assignment (figure 8.62)
- 8.7.3 Implementation using D-type flip-flops (figure 8.63, 64)

July 2000

Univ. of Stellenbosch - Digital Systems 144

318

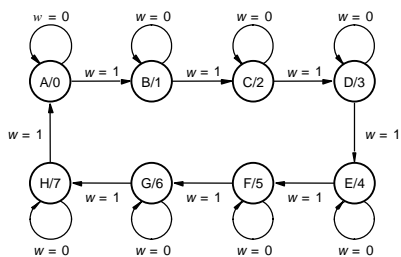

July 2000

Figure 8.60 State diagram for a counter

319

Present state	Next state		Output
	w = 0	w = 1	
A	A	B	0
B	B	C	1
C	C	D	2
D	D	E	3
E	E	F	4
F	F	G	5
G	G	H	6
H	H	A	7

July 2000

Figure 8.61 State table for the counter


320

	Present state $y_2 y_1 y_0$	Next state		Count $z_2 z_1 z_0$
		$w = 0$	$w = 1$	
		$Y_2 Y_1 Y_0$	$Y_2 Y_1 Y_0$	
A	000	000	001	000
B	001	001	010	001
C	010	010	011	010
D	011	011	100	011
E	100	100	101	100
F	101	101	110	101
G	110	110	111	110
H	111	111	000	111

July 2000

Figure 8.62 State-assigned table for the counter


321

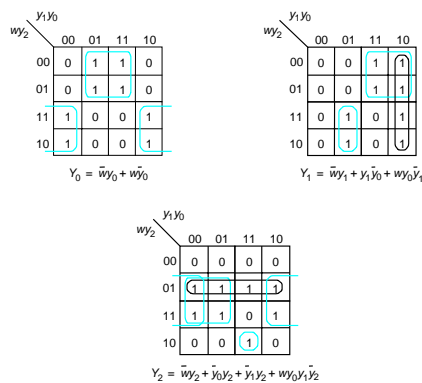

July 2000

Figure 8.63 Karnaugh maps for D flip-flops for the counter

322

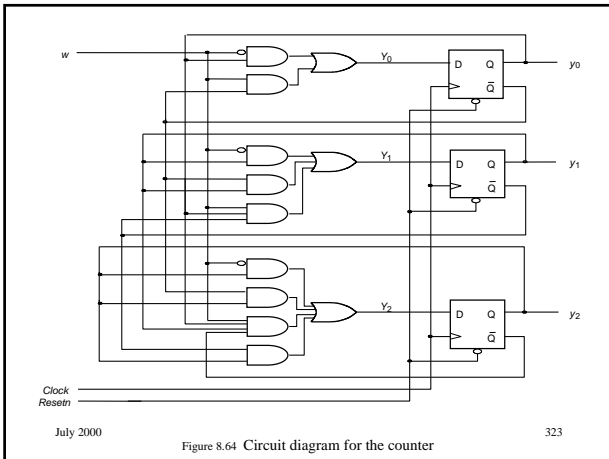

8.7.4 Implementation using JK-flip-flops

- JK properties
 - If present state = 0 and we want the next state = 0, then J = 0 and K = d.
 - If present state = 0 and we want the next state = 1, then J = 1 and K = d.
 - If present state = 1 and we want the next state = 1, then J = d and K = 0.
 - If present state = 1 and we want the next state = 0, then J = d and K = 1.

July 2000 324

Univ. of Stellenbosch - Digital Systems 144

- Implementation of counter with JK's in figures 8.65 – 8.67.
- Excitation table (figure 8.65) same as state assignment table.



July 2000 325


Univ. of Stellenbosch - Digital Systems 144

Present state $y_2y_1y_0$	Flip-flop inputs								Count $z_2z_1z_0$	
	$w = 0$				$w = 1$					
	$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0		
A	000	000	0d	0d	0d	001	0d	0d	1d	000
B	001	001	0d	0d	d0	010	0d	1d	d1	001
C	010	010	0d	d0	0d	011	0d	d0	1d	010
D	011	011	0d	d0	d0	100	1d	d1	d1	011
E	100	100	d0	0d	0d	101	d0	0d	1d	100
F	101	101	d0	0d	d0	110	d0	1d	d1	101
G	110	110	d0	d0	0d	111	d0	d0	1d	110
H	111	111	d0	d0	d0	000	d1	d1	d1	111

July 2000 326

Figure 8.65 Excitation table for the counter with JK flip-flops

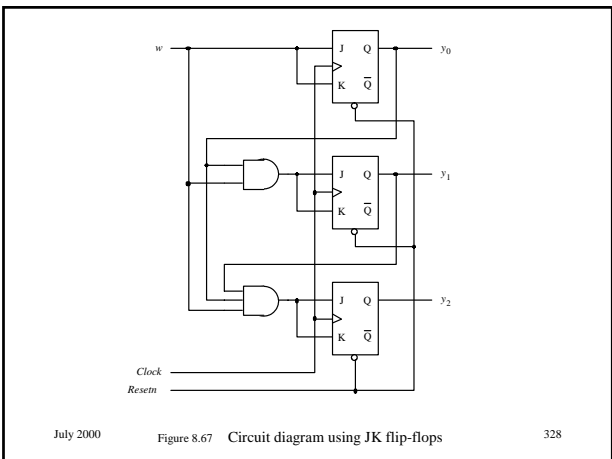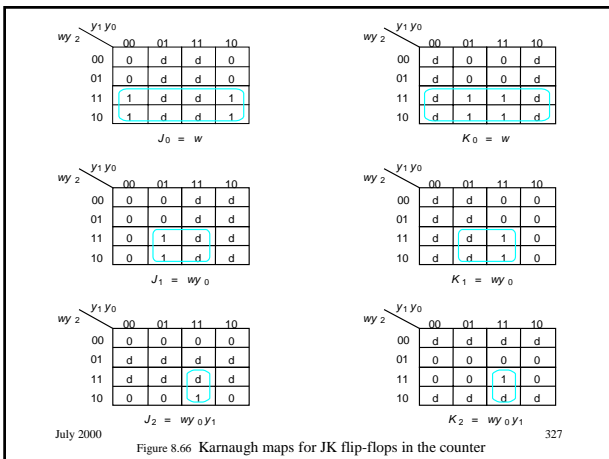

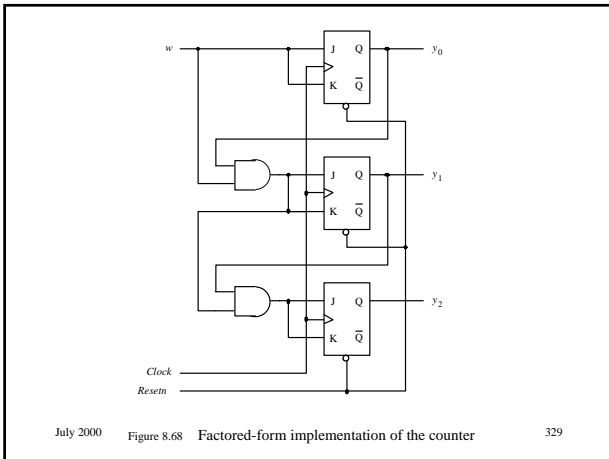

Other counters

- Any counter can be designed using state machine principles.
- The most important application of state machines is for the implementation of control circuits.
- Designing state machines in VHDL is a very powerful tool.

July 2000 Univ. of Stellenbosch - Digital Systems 144 330

The end!

July 2000 Univ. of Stellenbosch - Digital Systems 144 331