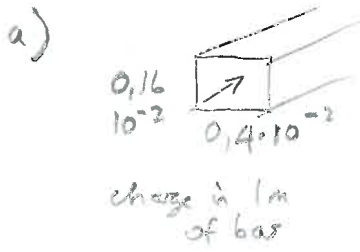


VRAAG 1




(X) $area = 0,4 \cdot 10^{-2} \times 0,16 \cdot 10^{-2} = 6,4 \cdot 10^{-4} m^2$ -6 X

$C/m^3 = \frac{1,6 \cdot 10^{-19}}{1 m^3} \cdot 10^{29} = 1,6022 \cdot 10^{10} C/m^3 (2)$

$C/m = 1,6022 \cdot 10^{10} \times 6,4 \cdot 10^{-4} = 10,254 \cdot 10^6 C/m (2)$ xL

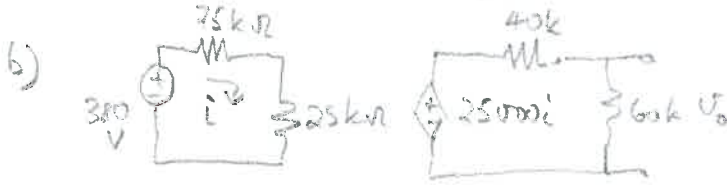
current $(\frac{C}{s}) = 10,254 \cdot 10^6 (\frac{C}{m}) \times 156,04 \cdot 10^{-6} (\frac{m}{s}) = 1600 A (2)$ 15,98 6



$i = \frac{380}{100k} = 3,8 mA$

$25000i = 3,8 \cdot 10^{-3} \cdot 25000 = 95V (2)$

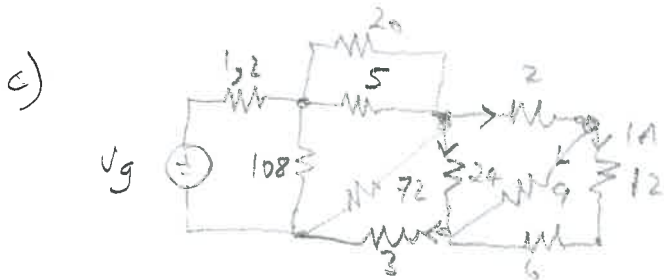$U_o = \frac{60k \cdot 95}{(40+60)k} = 57V (2)$ 4



Voltage across 9 ohm resistor

$V_q = 1(12+6) = 18V (2)$

Current in 9 ohm resistor = $\frac{18}{9} = 2A$

Current in 2 ohm resistor = $1+2 = 3A$

Voltage across 24 ohm resistor = $(2 \times 3) + 18V = 24V$

Current in 24 ohm resistor is $\frac{24}{24} = 1A$

Current in 3 ohm resistor is $i_{24} + i_9 + i_6 = 1 + 2 + 1 = 4A (2)$

voltage across 72 ohm = $24 + (3 \times 4) = 36V$

\therefore current in 72 ohm resistor = $\frac{36}{72} = 0,5 A (2)$ 6

d) To work out power delivered, work out total circuit resistance:

$(12+6) \parallel 9 = 6$; $(2+6) \parallel 24 = 6$; $(6+3) \parallel 72 = 8$

$8 + (20 \parallel 5) = 12$; $12 \parallel 108 = 10,8$; $1,2 + 10,8 = 12 \Omega (2)$

Power $P_3 = \frac{6^2}{12} = 3W (2)$ 4

a) At middle node

$$\frac{V_{xc} - 150}{25} + \frac{V_x}{80} + \frac{V_x - (150 - 15I_{sc})}{40} = 0 \quad (i)$$

$$I_x = \frac{150 - V_x}{25} \quad (ii) \quad (4)$$

$$(ii) \rightarrow (i) \times 80 \quad 3.2 V_x - 480 + V_x + 2V_x - 300 + \frac{30}{25} (150 - V_{sc}) = 0$$

$$5V_{sc} - 600 = 0$$

$$V_{sc} = 120$$

(3)

[7]

b) Three mesh equations:

$$50 = 5(I_1 - I_2) + 20(I_1 - I_3) \quad (i)$$

$$0 = 5(I_2 - I_1) + 1I_2 + 4(I_2 - I_3) \quad (ii)$$

$$0 = 20(I_3 - I_1) + 4(I_3 - I_2) + 15I_3 \quad (iii)$$

$$\text{constraint} \quad I_x = I_1 - I_3 \quad (iv)$$

(4)

$$(iv) \rightarrow (iii) \quad 0 = 20I_3 - 20I_1 + 4I_3 - 4I_2 + 15I_1 - 15I_3$$

$$0 = -5I_1 - 4I_2 + 9I_3 \quad (v)$$

$$\text{so} \quad 50 = 25I_1 - 5I_2 - 20I_3$$

$$0 = -5I_1 + 10I_2 - 4I_3$$

$$0 = -5I_1 - 4I_2 + 9I_3$$

(4)

[8]

c) Thevenin voltage between a and b? Just DC voltage across 33 Ω

$$V_{ab} = 150 - 15I_x = 150 - \frac{15(150 - 120)}{25} = 132V \quad (2)$$

Mean we will meter or oscilloscope

Put SC between a and b and measure

current I_{sc} .


$$\text{then } R_{th} = \frac{V_{ab}}{I_{sc}}$$

(3)

[5]

Übung 2

b) $I_2 = I_x$

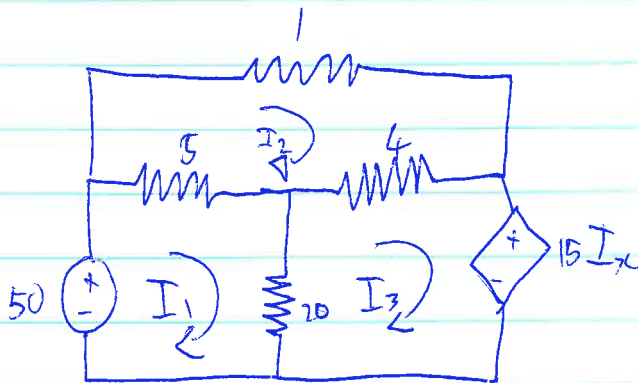

$$50 = 5(I_1 - I_2) + 20(I_1 - I_3)$$

$$I_2 + 4(I_2 - I_3) + 5(I_2 - I_1) = 0$$

$$20(I_3 - I_1) + 4(I_3 - I_2) + 15I_2 = 0$$

$$50 = 25I_1 - 5I_2 - 20I_3$$

$$0 = -5I_1 + 10I_2 - 4I_3$$

$$0 = -20I_1 + 11I_2 + 24I_3$$


zwei Sol.:

$$20(I_3 - I_1) + 4(I_3 - I_2) + 15I_2 = 0$$

~~$-20I_1 + 24I_3$~~

$$-20I_1 - 4I_2 + 24I_3 = -15I_2$$

VRAAG 3

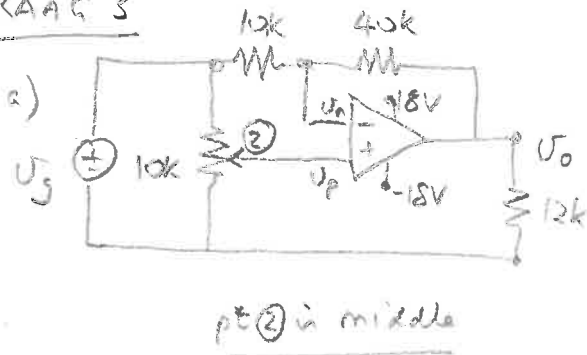

pt 2 in middle

$$U_n = U_p = U_g / 2 \quad (2)$$

$$\begin{aligned} &\times 1000 \rightarrow \text{mV} \\ &\text{(at node)} \quad \frac{U_n - U_g}{10} + \frac{U_n - U_o}{40} = 0 \end{aligned} \quad (2)$$

$$4(U_n - U_g) + U_n - U_o = 0$$

$$4\left(\frac{U_g}{2} - U_g\right) + U_n = U_o$$

$$U_o = -\frac{3}{2} U_g \quad (2)$$

$$U_g = 10V : U_o = -15V \quad (i)$$



$$U_g = 2V : U_o = -3V \quad (ii) \quad [8]$$

$$(i) P_{12k} = \frac{-15^2}{12k} = 18,75 \text{ mW}$$

$$(ii) P_{12k} = \frac{-3^2}{12k} = 0,75 \text{ mW}$$

must get right values & give units

[4]

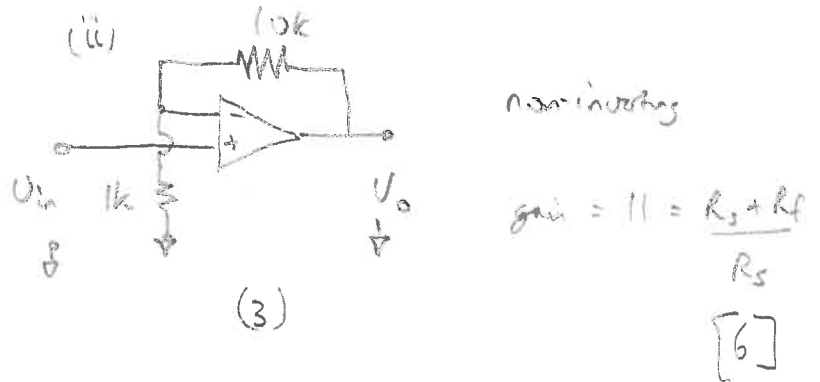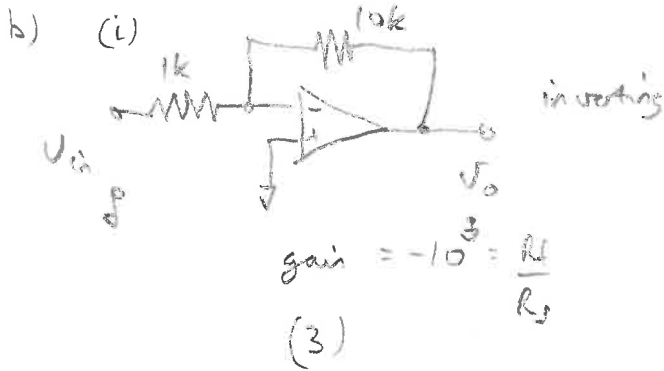

c) Input resistance of :

$$(i) \text{ as } U_n = 0$$

$$R_{in} = 1k \Omega$$

(1)

$$(ii) \text{ as } U_p \rightarrow U_n \text{ resistance} = \infty \Omega$$

for ideal op amp

$$R_{in} = \infty \Omega$$

(1)

[2]

VRAAG 4

$$a) \quad i = \frac{400 \cdot 10^{-3}}{5 \cdot 10^{-6}} t = 80 \cdot 10^3 t \quad 0 \leq t \leq 5 \mu s$$

$$i = 400 \cdot 10^{-3} \quad 5 \leq t \leq 20 \mu s$$

$$i = \frac{300 \cdot 10^{-3}}{30 \cdot 10^{-6}} t - 0,5 = 10^4 t - 0,5 \quad 20 \leq t \leq 50 \mu s. \quad (3)$$

$$q = \int_0^{5 \cdot 10^{-6}} 8 \cdot 10^4 t \, dt + \int_{5 \cdot 10^{-6}}^{20 \cdot 10^{-6}} 0,4 \, dt$$

$$= 8 \cdot 10^4 \left. \frac{t^2}{2} \right|_0^{5 \cdot 10^{-6}} + 0,4 \left(15 \cdot 10^{-6} \right) \quad (2)$$

$$= 4 \cdot 10^4 (25 \cdot 10^{-12}) + 6 \cdot 10^{-6}$$

$$\underline{q = 7 \mu C.} \quad (1)$$

[6]

$$b) \quad U = \frac{1}{C} \int_0^{t_1} i \, dt + \frac{1}{C} \int_{t_1}^{t_2} i \, dt + 0 \quad i = C \frac{dv}{dt} \quad \checkmark$$

$$= 2,128 \cdot 10^6 \int_0^{5 \cdot 10^{-6}} 8 \cdot 10^4 x \, dx + 2,128 \cdot 10^6 \int_{5 \cdot 10^{-6}}^{20 \cdot 10^{-6}} 0,4 \, dx \quad \checkmark$$

$$= 2,128 \cdot 10^6 \left[8 \cdot 10^4 \frac{x^2}{2} \Big|_0^{5 \cdot 10^{-6}} + 0,4 x \Big|_{5 \cdot 10^{-6}}^{20 \cdot 10^{-6}} \right] \quad \checkmark$$

$$= 2,128 \cdot 10^6 \left[4 \cdot 10^4 (25 \cdot 10^{-12}) + 0,4 (15 \cdot 10^{-6}) \right]$$

$$\quad (10^{-6}) \quad + (6 \cdot 10^{-6})$$

$$\underline{U = 14,9 V}$$

[4]